

TOM ESSENPREIS — KB9ENS

# MAGNETIC LOOP ANTENNA

# OVERVIEW



- Why?
- Circuit
- Calculator
- Hands On
- Demo

## WHY?

- Acquisitions: (Pick two)
  - Cost/Schedule/Performance
- Antennas: (Pick two)
  - Small Size (relative to wavelength)
  - Efficiency
  - Broadband
- Noise rejection?



# CIRCUIT:

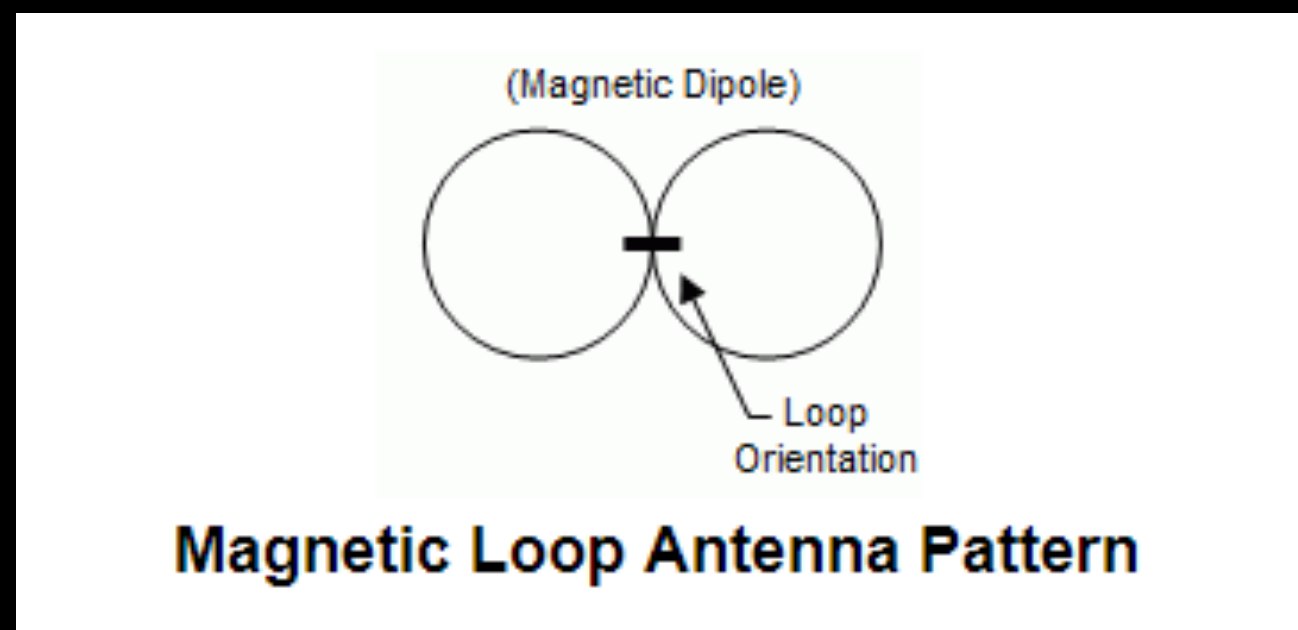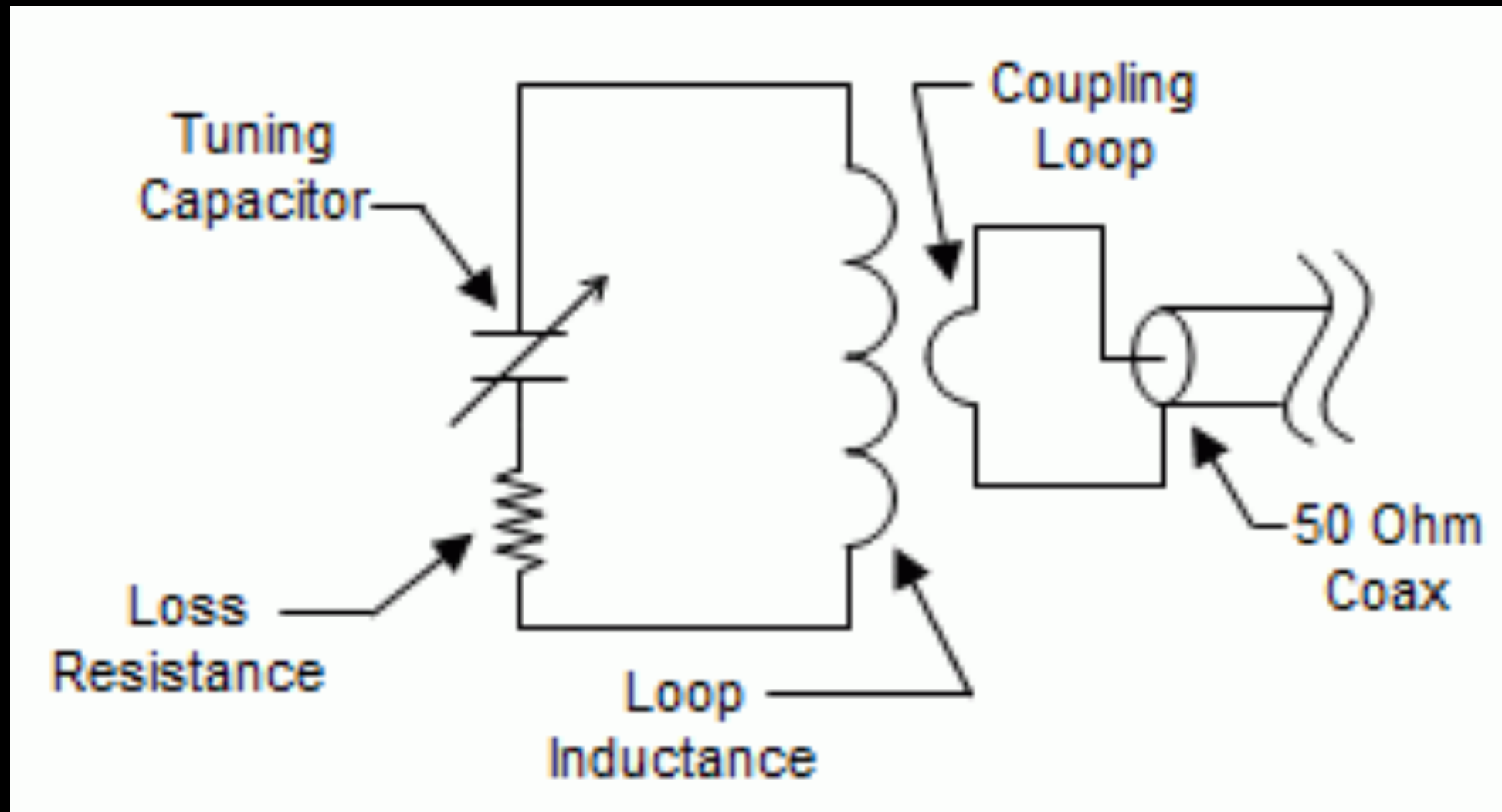

# CALCULATOR

- ARRL Antenna manual
- AA5TB Calculator

## Small Loop Equations for a Copper Loop

*(circular loop assumed, results may vary with other shapes)*

Radiation Resistance, Ohms:  $RR = (3.38 \times 10^{-8})(f^2 A)^2$

Loss Resistance, Ohms:  $RL = (9.96 \times 10^{-4})(\sqrt{f})(S/d)$

Efficiency:  $\eta = RR/(RR+RL)$

Inductance, Henrys:  $L = (1.9 \times 10^{-8})S[7.353 \log_{10}(96S/\pi d) - 6.386]$

Inductive Reactance, Ohms:  $XL = 2\pi f(L \times 10^6)$

Tuning Capacitor, Farads:  $CT = 1/2\pi f(XL \times 10^6)$

Quality Factor:  $Q = (f \times 10^6)/\Delta f = XL/2(RR + RL)$

Bandwidth, Hertz:  $\Delta f = (f \times 10^6)/Q = [(f_1 - f_2) \times 10^6]$

Distributed Capacity, pF:  $CD = 0.825$

Capacitor Potential, Volts:  $VC = \sqrt{PXLQ}$

Capacitor Voltage Rating: 75,000V/in

where

$f$  = operating frequency, MHz

$A$  = area of loop, square feet

$S$  = conductor length, feet

$d$  = conductor diameter, inches

$\eta$  = decimal value;  $dB = 10 \log_{10} \eta$

$P$  = transmitter power, Watts



# Small Magnetic Loop Antenna Calculator ver. 1.22a

by Steve Yates

AA5TB

[aa5tb@yahoo.com](mailto:aa5tb@yahoo.com)

Updated April 28, 2009

Input the following parameters:

Design Frequency =	14.200 MHz	
Loop Diameter =	3.500 feet	1.067 m
Conductor Diameter =	0.750 inches	19.050 mm
Added Loss Resistance =	0.000 milliohms	
RF Power =	10.000 Watts	


Calculated Results:

Bandwidth =	21.181 kHz (-3 dB points)	
Efficiency =	69.806 %	-1.561 dB
Loop Area =	9.621 ft <sup>2</sup>	0.894 m <sup>2</sup>
Radiation Resistance =	127.210 mΩ	
Total Loss Resistance =	55.025 mΩ	
Loop Circumference =	10.996 ft	3.351 m
Wavelength Percentage =	15.874 % λ	
Loop Inductance =	2.739 μH	
Distributed Capacitance =	9.016 pF	
Q (Quality Factor) =	670.412	
Tuning Capacitor =	45.870 pF	
Capacitor Voltage =	1279.891 V	
Minimum Plate Spacing =	17.065 mils (1/1000 in)	0.433 mm

Notes:

1. To truly be considered a small loop, the **Loop Circumference** should be less than 10 % λ. Larger loops will have greater efficiency but smaller nulls.
2. To see the effects of bad joints, etc., input realistic values into the **Added Loss Resistance** box.
3. The sheets are protected to prevent the user that is unfamiliar with Excel from accidentally corrupting formulas. To unlock the sheets use the password **aa5tb**.
4. This application is free to use as you wish. If you modify it and pass it on all that I ask is that you give me credit for my part of the work. Thanks!

## Loop Performance

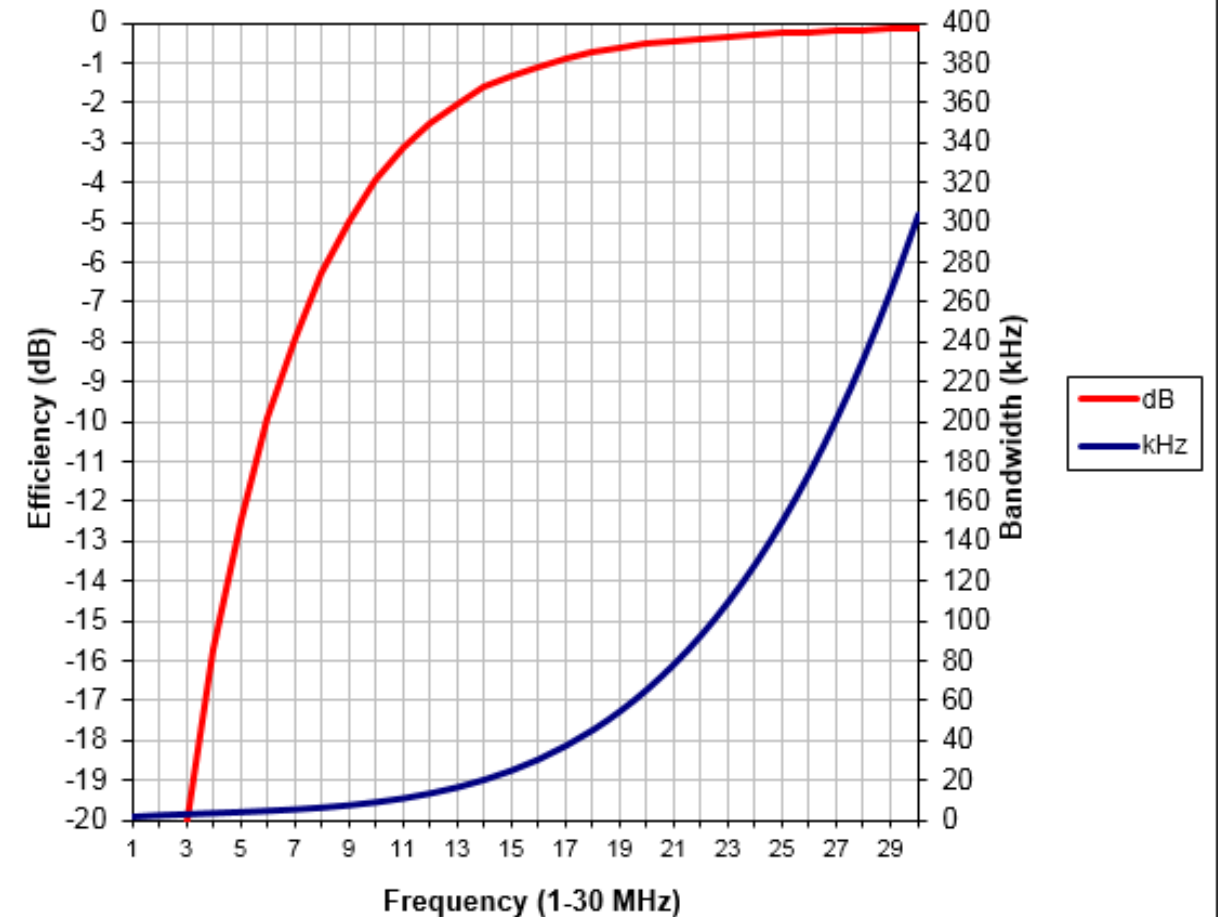

# HANDS ON

- Volunteers:
  - Analyzer
  - Capacitor
- Exercise
  1. Bound the performance
  2. Tune a specific frequency
  3. Attach transceiver and tune for sound
  4. Test!



# QUESTIONS

